team05_lab2_report

b08901056 盧弘偉 b08901069 黃政勛 b08901175 郭柏言


層級架構

```
DE2_115


Rsa256Core.SV

Rsa256Wrapper.SV
```


FSM - Wrapper

 


Block Diagram - Wrapper

 


FSM - Core

 

Three counters for states change control.

 


 Three 256-1 MUX select i'th bit of d, t, and m.




Register m_mont_1 caculate (m*t*2^-256) mod i_n.

 Register m_mont_2 caculate (t*t*2^-256) mod i_n. (both during state = S_MONT)



Initial t to (i_a*2^256) mod i_n , and set m to 1 when state = S_PREP.

 Update t & m to m_mont_2 & m_mont_1 when state = S_CALC.



Fitter Summary

Fitter Summary	
Fitter Status	Successful - Wed Mar 23 14:07:30 2022
Quartus II 64-Bit Version	15.0.0 Build 145 04/22/2015 SJ Full Version
Revision Name	DE2_115
Top-level Entity Name	DE2_115
Family	Cyclone IV E
Device	EP4CE115F29C7
Timing Models	Final
Total logic elements	7,556 / 114,480 (7 %)
Total combinational functions	7,401 / 114,480 (6 %)
Dedicated logic registers	2,199 / 114,480 (2 %)
Total registers	2199
Total pins	518 / 529 (98 %)
Total virtual pins	0
Total memory bits	0 / 3,981,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 532 (0 %)
Total PLLs	1 / 4 (25 %)

Timing Analyzer

TimeQuest Timing Analyzer Summary

Quartus II Version Version 15.0.0 Build 145 04/22/2015 SJ Full Version

Revision Name DE2_115

Device Family Cyclone IV E

Device Name EP4CE115F29C7

Timing Models Final

Delay Model Combined

Rise/Fall Delays Enabled

Unconstrained Paths			
	Property	Setup	Hold
1	Illegal Clocks	0	0
2	Unconstrained Clocks	0	0
3	Unconstrained Input Ports	0	0
4	Unconstrained Input Port Paths	0	0
5	Unconstrained Output Ports	1	1
6	Unconstrained Output Port Paths	1	1

遇到的問題與解決辦法

- 1. 剛寫完 Core 時跑 testbench 發現答案有錯, 怎麼 debug 都找不出問題, 後來跟隔壁組對答案才發現我們的 testbench 給的 gold 是錯的, 用他們的 tb 跑也是錯的(直接跟他們要了tb_verilog 整個資料夾換掉), 但把我們的Core 拿去他們工作站跑卻是對的, 目前還沒找出原因, 猜測是 tb 把 dec 讀進來時編碼有問題導致結果不一樣。
- 2. 寫完 Core 和 Wrapper 之後跑 testbench 都成功, Quartus 編譯、燒錄也成功, 但執行 python 時卻發現 FPGA 沒有傳東西回來(但應該有輸入測資)。後來我們修改Wrapper, 在 wait_calculate 這個 state 讓 avm_read, avm_write 皆為 0 就修好了(原本是讓他 read RX_status)。我們認為可能是因為RS232 protocol 在沒有要讀東西時不能亂把 avm_read 設成 1, 但 testbench 並沒有規範這件事。